







Achieving Fractional-ppm Ratio Precision with Two-Stage Transformers

For the purpose of providing precise ratios, nothing has yet exceeded the precision of the ratio transformer, in which the number of turns wound on a core is absolutely invariant with respect to almost everything short of destruction of the device. However, ratio transformers are subject to errors that can be reduced, by means of two-core transformer circuits, to facilitate AC comparisons to one-part-in-10⁹ precision.

BY HENRY P. HALL, GENERAL RADIO COMPANY

Advances in low-frequency AC measurement techniques during the past two decades have made part-permillion comparisons of voltage, current, and impedance commonplace. This order of precision depends largely upon the accuracy and stability of ratio transformers. Although engineers regard transformers as crude, non-linear, lossy, frequency-dependent devices that are unstable with respect to temperature and shock—as, indeed, they are—nonetheless, properly designed transformers can establish more precise voltage or current ratios than any other known device.

Recently, the precision realized in AC comparisons has far exceeded 1 ppm, and may even be as great as one part in 10⁹. Such precision has been made possible, in large part, by the use of two-core transformer circuits—commonly referred to as "two-stage" transformers. We shall discuss three such circuits here. However, before one can appreciate them fully, it is necessary to understand the sources of error in the corresponding connections of a simple, single-core transformer. Moreover, to evaluate the errors in "two-stage" circuits, it is necessary to develop a systematic method of handling multi-winding transformers algebraically.

Single-Core Transformer Connections

Of the many possible ways in which transformers can be connected, the three configurations that are of the most importance for precision measurements are shown in Fig. 1. The first (1a) provides isolation, a precise ratio between primary and secondary, and inversion—if desired. Among some of its particular applications are provision of the "bootstrap" voltage used in ratio determinations [1], injection of balancing voltages in null circuits [1, 2], and leadimpedance compensation in four-terminal bridges [3, 4].

The second (1b) is a step-down autotransformer or transformer divider. It is used to provide a precise voltage ratio, E_2/E_s , or to provide two arms of an impedance bridge [6, 7] that requires an accurate ratio of E_1/E_2 . Note that the windings are aiding.

The third connection (1c) uses three windings, but usually only the ratio E_1/E_2 must be precise. Voltages E_1 and E_2 may drive impedances Z_1 and Z_2 in a comparison bridge. This circuit is commonly used for high-impedance measurements [6, 8].

Although we shall discuss voltage ratios, we could discuss current ratios just as well. Since a linear passive network is reciprocal, the open-circuit voltage ratio in one direction is equal to the short-circuit current ratio in the other. (That is, for inputs E_1 and I_2 , respectively, $E_{20C}/E_1 = I_{18C}/I_2$). Because transformers are non-linear, the numerical value of these ratios depends upon the flux level, which is usually very low in shorted transformers. However, the algebraic expressions presented below are valid for either voltage or current ratios at any flux level. Passive null networks containing transformers can be used with input (source) and outpur (detector) interchanged (which converts voltage ratios into current ratios, and vice versa), as a long as core saturation is avoided. They are usually designed, however, to provide optimum performance with a specific connection.

Two-Winding Equivalent Circuits

A passive three-terminal network can be represented as an equivalent T network. A useful T-network representation of a transformer is presented in Fig. 2. The two windings have a common connection; however, an ideal 1:1 transformer can be added if winding isolation is desired. Two sets of signs are given for the impedances. The upper set applies to the non-inverting connection, and the lower to the inverting connection. In this circuit Z_{12} is the mutual impedance, E_2/I_1 . (Note that, by reciprocity, $Z_{12} = Z_{21}$.) Z_{12} is the "sloppy" parameter of a transformer, that varies widely with level, frequency, and almost everything else. It is shown as a mutual inductance, and a parallel resistance representing core loss. While a series combination is sometimes easier to use (the series values can be obtained by a parallel-to-series conversion), the parallel arrangement approximates more closely the actual physical behavior of an iron-core device.

 N_1 and N_2 represent exact numbers of turns, and are, therefore, whole numbers that remain absolutely constant (unless turns are added or removed). We can arbitrarily set N_1 and N_2 to exact numbers, because only three quantities are required to describe the network of Fig. 2 (at a particular level, frequency, etc.). We have five— Z_{12} , z_1 , z_2 , N_1 , and N_2 —and thus have two to play with. Each arm includes an impedance that is a function of the mutual impedance, multiplied by functions of the numbers of turns. The ratio of these two impedances is exact, and the ratio of inductance to resistance is the same in both.

By definition, the "leakage" or "winding" impedances, z_1 and z_2 , are those additional impedances that are required in

Editor's Note:

Although the theoretical ratio established by a ratio transformer is precisely determined by the (integral) number of turns that each of its windings make around its core(s), in a practical sense it is subject to errors that arise because of winding resistance, leakage inductance, etc. Transformers employing two separate cores ("two-stage" transformers) have been devised to minimize some of these errors for various applications. In this article, Mr. Hall presents a logical development of the techniques that have been used to reduce ratio-transformer errors, and evaluates the errors for a number of circuit configurations. the arms of the T network to produce the correct values of the transformer terminal impedances. That is, z_1 and z_2 are defined by

$$z_1 = Z_{11} - \left(\frac{N_1}{N_2}\right) Z_{12} \text{ and } z_2 = Z_{22} - \left(\frac{N_2}{N_1}\right) Z_{12}$$
 (1)

where Z_{11} and Z_{22} are the open-circuit impedances at the terminals. The components of z_1 and z_2 have physical significance if N_1 and N_2 are the actual numbers of turns (which may differ from the nominal or design values). The resistances, r_1 and r_2 , are the respective resistances of the windings themselves, and are very nearly equal to the DC resistance of the wire. (At high frequency their values are increased somewhat by skin and proximity effects.) The inductances, l_1 and l_2 , are the respective leakage inductances, due to flux that cuts one winding and not the other. These impedances are linear, and are relatively frequency 10 dependent.

The equivalent circuit of Fig. 2 does not show distributed capacitance between windings, or between the windings and the core or any shields that may be used. The effect of distributed capacitance can be very difficult to calculate but, to a first approximation, it can be represented by lumped capacitances between the terminals. Alternatively, these capacitances can be regarded as changing the effective values of z_1, z_2 , and Z_{12} , so that the equivalent circuit can be used.

In Fig. 1a, loading capacitance can improve the ratio accuracy of the circuit near the resonant frequency, but above this frequency the accuracy is degraded quickly. In balanced circuits (Figs. 1b and 1c) the capacitance balance, which is important, can be improved by means of external trimming capacitors.

Errors in Simple Transformers

Using the equivalent circuit of Fig. 2, we can easily calculate the ratios of interest in the circuits of Fig. 1. For the first circuit (Fig. 1a)

$$\frac{E_2}{E_1} = \frac{\frac{N_2}{N_1}}{1 + \frac{N_2 z_1}{N_1 Z_{12}}} \approx \frac{N_2}{N_1} \left[1 - \frac{N_2}{N_1} \left(\frac{r_1}{R_{12}} + \frac{l_1}{M_{12}} + \frac{r_1}{j\omega M_{12}} + \frac{j\omega l_1}{R_{12}} \right) \right] \quad (2)$$

Note that in Fig. 2, the set of signs to be used depends upon the connection. The lower set of signs corresponds to a voltage inversion, and would add a minus sign to equation (2). If z_1/Z_{12} were large, the voltage ratio would be imprecise, and would vary widely as Z_{12} varied with level, frequency, etc. However, by means of proper design, these error terms can be made very small so that, despite large changes in Z_{12} , the ratio remains precise.

 M_{12} is proportional to N², while l_1 and l_2 increase less rapidly as turns are added, and are approximately proportional to N if a twisted pair of wires is used. Likewise, R_{12} is proportional to N², while r_1 and r_2 are proportional to N for a given wire size. Therefore, many turns of heavy wire produce a good ratio. M_{12} is also proportional to the permeability of the core—and cores with values of μ as great as 100 000 or more are not uncommon. Since R_{12} (parallel) is increased as core losses are reduced, very thin iron is used to reduce eddy-current losses.

Because of the symmetry of their magnetic fields, toroidal cores are usually used in precision transformers. While accurate ratios are possible with cores of other shapes, flux tends to cut across sharp corners, thereby failing to link some wires, which results in increased leakage inductance. Moreover, the relatively large "window" area of a toroid affords a large space for the windings, without placing them too far from the core.

The circuit of Fig. 1a, corresponding to equation (2), produces the poorest ratio accuracy of the three because one winding carries current and the other doesn't. The error is simply a result of the voltage drop, Iz_1 . Using twisted windings, 1:1 ratios within about 100 ppm are common. Ratios other than 1:1 produce greater errors, due to higher leakage inductance caused by poorer winding geometry.

In the divider circuit of Fig. 1b, the mutual impedance becomes negative, as shown in the equivalent circuit of Fig. 3. For this connection

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} \left[\frac{1 + \frac{z_1 N_2}{Z_{12}(N_1 + N_2)}}{1 + \frac{z_2 N_1}{Z_{12}(N_1 + N_2)}} \right]$$
$$\approx \frac{N_1}{N_2} \left[1 + \left(\frac{N_1 N_2}{Z_{12}(N_1 + N_2)} \right) \left(\frac{z_1}{N_1} - \frac{z_2}{N_2} \right) \right]$$
(3)

$$\begin{split} & \frac{E_2}{E_s} = \frac{N_2}{N_1 + N_2} \left[\frac{1 + \frac{z_2 N_1}{Z_{12} (N_1 + N_2)}}{1 + \frac{(z_1 + z_2) N_1 N_2}{Z_{12} (N_1 + N_2)^2}} \right] \\ & \approx \frac{N_2}{N_1 + N_2} \left[1 + \left(\frac{N_1 N_2}{Z_{12} (N_1 + N_2)} \right) \left(\frac{z_2}{N_2} - \frac{z_1 + z_2}{N_1 + N_2} \right) \right] (4) \end{split}$$

Here all of the error terms include winding impedance *differences*, so that with careful design, the ratios can be made much better than those of the unsymmetrical circuit of Fig. 1a. At low frequencies the winding *resistance* becomes important. (At DC, the circuit would become simply a resistance divider.) Equations (3) and (4) indicate that the resistance per turn should be equal for both halves of the divider; therefore, both windings should use the same size wire, regardless of the number of turns. Wire from the same spool is often specified, to ensure uniformity of wire size. A good leakage-inductance balance is obtained easily for 1:1 transformers if a twisted pair is used. For other ratios, a bundle of wires is wound. For example, a 10:1 ratio would use a bundle of eleven wires, with ten of them connected in



• Experimental model of a multiple-ratio, two-stage transformer, wound on two 2½-inch-diameter cores. Referring to Fig. 4, which shows a schematic representation of this transformer, winding a is on the bottom core only. The other two windings consist of a twisted pair that is wound on both cores simultaneously. One wire of the pair comprises windings b and d, and the other, windings c and f. If winding a is disconnected, the unit becomes a simple transformer (wound on two cores) in which the in-phase 1:1 ratio error at a frequency of 1 kHz and a level of 25 V was measured as 80 ppm. With winding a connected, which makes the unit a two-stage transformer, the corresponding in-phase 1:1 ratio error becomes approximately 0.05 ppm.



Fig. 1. The three most important transformer configurations for precision measurement application: (a) simple transformer, that provides isolation, precise ratio, and inversion—if desired; (b) step-down autotransformer, or transformer divider, that provides precise ratio; (c) three-winding transformer that provides precise r_1/E_2 ratio, and is commonly used for high-impedance measurements.





series to form one winding. By means of such precautions, in addition to the use of high-permeability cores, 1:1 ratios within 0.1 ppm at optimum frequency are not difficult to realize, and 10:1 ratio accuracy can be almost as good.

Figure 1c shows a three-winding circuit, for which an exact solution requires the multi-winding theory that follows. However, in this relatively simple case it is evident that the open-circuit ratio, E_1/E_2 , is simply the ratio of the mutual impedances of windings N_1 and N_2 to the input winding, N_3 . This ratio is independent of the secondary-winding impedances. A perfect ratio would result if both output windings were linked by the same flux. Therefore, the symmetry of the windings and the magnetic field is the limiting factor, and extremely accurate open-circuit ratios, approaching 0.001 ppm, are possible.

Although the impedance of the output windings does not affect the open-circuit ratio, in the bridge circuit (shown dashed), the output impedance of each winding is in series with one of the impedances being compared. These output impedances are the leakage impedances of the output windings with respect to each other $(z_{12} \text{ and } z_{21})$.

The Three-Winding Transformer

Since a three-winding transformer is a passive, three-port network, we can write the equations

$$E_1 = I_1 Z_{11} + I_2 Z_{12} + I_3 Z_{13}$$
(5)

$$E_2 = I_1 Z_{21} + I_2 Z_{22} + I_3 Z_{23} \tag{6}$$

$$E_3 = I_1 Z_{31} + I_2 Z_{32} + I_3 Z_{33} \tag{7}$$

Due to reciprocity:

 $Z_{12} = Z_{21}; Z_{13} = Z_{31};$ and $Z_{23} = Z_{32}$ (at the same level, frequency, etc.).

Moreover, each pair of windings can be considered as a two-winding transformer, so that the equivalent circuit of Fig. 2 applies. Therefore, the input impedance, Z_{11} , can be written in either of two ways, depending upon which other winding is considered as the output winding.

$$Z_{11} = z_{12} + \frac{N_1 Z_{12}}{N_2}$$

$$Z_{11} = z_{13} + \frac{N_1 Z_{13}}{N_2}$$
(8)

In equation (8), the leakage impedances have been given two subscripts. This notation is taken to mean that, in general, \mathbf{z}_{1k} is the leakage of winding j with respect to winding k. Thus, winding 1 has two values of leakage impedance z_{12} and z_{13} . The real parts of these impedances, r_{12} and r_{13} , are very nearly equal because both are very nearly the resistance of the *same* piece of wire. However, l_{12} and l_{13} may be quite different. If windings 1 and 2 were a twisted pair on a long rod, with winding 3 located some distance away, it is easy to see that l_{12} would be much smaller than l_{13} . Even when a toroidal core is used, there will be some difference between the two quantities—particularly if the windings are on different layers or on different sections of the core.

Likewise, the open-circuit impedances of the other two windings can each be expressed in two ways:

$$Z_{22} = z_{21} + \frac{N_2 Z_{12}}{N_1}$$

$$Z_{22} = z_{23} + \frac{N_2 Z_{23}}{N}$$
(9)

or

or

$$z_{31} = z_{31} + \frac{N_3 Z_{13}}{N}$$

 Z_3

or

$$Z_{33} = z_{32} + \frac{N_3 Z_{23}}{N_2}$$

(10)

Equations (8), (9), and (10) are useful in reducing network equations to a more meaningful form.* Together with the preceding equations, they present a complete picture of a three-winding transformer. The extension of this system to transformers with even more windings is obvious, but one should be warned that the calculations can become very tedious.

The Brooks and Holtz Two-Stage Transformer [9, 2]

Figure 4 shows a circuit that provides an accurate isolated voltage ratio (cf Fig. 1a). It was originally used to achieve an accurate current ratio, for use in a more accurate wattmeter. However, by reciprocity, if it can provide a good current ratio, then it can also provide a good voltage ratio.

In Fig. 4, the circuit is shown as a voltage-ratio device. One way to consider it is as a feedback network. The full input voltage is applied to winding a. As a result, a voltage appears across winding c that is slightly smaller than N_2E_1 / N_1 by the error factor of equation (2). This error results from the voltage drop across the winding resistance and leakage inductance, caused by the magnetizing current. The open-circuit voltage in winding b would also be low, due to this same type of error, but it would be slightly different if the coupling between windings a and b differed from that between windings a and c (i.e., $Z_{ab} \neq N_1 Z_{ac}/$ N2). The difference between the input voltage and the "feedback" voltage across winding b is applied to a second transformer, which adds a voltage proportional to this difference to the output. (Actually, winding b does carry some current, so that its voltage is not the true open-circuit voltage-but this current is usually very small).

Another way to look at this circuit is simply to say that winding a supplies the magnetizing current to establish the flux in transformer T_1 , and the remaining windings become two transformers with their primaries and secondaries connected in series. Since they carry very little current, these windings introduce little error. This viewpoint makes the circuit more similar to the other two-stage circuits that will be described.

Referring to Fig. 4, the open-circuit voltage ratio, E_2/E_1 , is approximately

$$\frac{E_2}{E_1} \approx \frac{N_2}{N_1} \left[1 - \left(\frac{N_2^2}{N_1^2}\right) \left(\frac{z_{ab}(z_{bc} + z_{df})}{Z_{ac}Z_{df}}\right) + \left(\frac{N_2}{N_1}\right) \left(\frac{z_{ab} - z_{ac}}{Z_{ac}}\right) \right]$$
(11)

The first error term is analogous to the error term of equation (2), but it is multiplied by a factor that makes it extremely small.

The second term is due to imperfect sampling—i.e., the feedback voltage on winding b is not necessarily produced by *exactly* the same flux that links winding c, because the coupling may be different. Although this term is very small, it can be larger than the first term. An experimental 10:1 transformer, using toroidal cores, exhibited a ratio error of

*From these equations one can derive the interesting and sometimes useful relationship:

$$\frac{z_{12} - z_{13}}{N_1^2} + \frac{z_{23} - z_{21}}{N_2^2} + \frac{z_{31} - z_{32}}{N_3^2} = 0$$







approximately 0.1 ppm (0.01 ppm of the input).

This two-stage transformer can also be represented by the equivalent T network of Fig. 2, if the constants of Fig. 2 are replaced by:

$$z_1 \approx z_{\rm ac} - z_{\rm ab} + \left(\frac{N_2}{N_1}\right) \left(\frac{z_{\rm ab}(z_{\rm bc} + z_{\rm df})}{Z_{\rm df}}\right)$$
(12)

$$z_2 \approx z_{\rm eb} + z_{\rm fd} + \left(\frac{N_2}{N_1}\right)^2 (z_{\rm ba} + z_{\rm d\,f})$$
 (13)

$$Z_{12} \approx Z_{ac} + \frac{N_2}{N_1} z_{ab} \approx Z_{ac}$$
(14)

Note that the effective primary-winding impedance, z_1 , is very small, but the secondary-winding impedance, z_2 , is increased by the transformed impedance of the primary circuit, so that the power efficiency is not improved.

This two-transformer network, as well as those yet to be discussed, can be constructed as a single, two-core device. Because windings b and d have the same number of terms, they can consist of a single winding on two cores. Similarly, windings c and f can comprise a single winding on two cores. To construct this transformer, winding a would be placed on one core, a second core added, and then the other windings placed on both cores.

The Two-Stage Divider [10]

Returning to Fig. 1b, the divider errors are caused by unequal voltage drops across the winding impedances. These errors could be reduced if the current could be reduced. The circuit shown in Fig. 5 might be tried for this purpose, with the intent that the added winding supply the magnetizing current. Although winding *a* does supply some magnetizing current, nonetheless the total current would divide between the two paths, depending upon the winding impedances, and the improvement would not be substantial. However, if large impedances of the proper ratio were added in series with windings b and c, thereby limiting the current in these windings to a small value, then winding a would have to supply most of the magnetizing current.

The most accurate way to add impedances of the correct ratio is by means of a second transformer divider with the same turns ratio, as shown in Fig. 6. Although this adds additional winding impedances that would, in themselves, tend to degrade the ratio, the current reduction is so substantial that the effect of winding-impedance unbalance can be extremely small.

The calculated approximate ratios for this device are

$$\frac{E_{1}}{E_{2}} \approx \frac{N_{1}}{N_{2}} \left[1 + \frac{z_{ac} - z_{ab}}{Z_{aa}} + \left(\frac{N_{1}N_{2}(N_{1}z_{ab} + N_{2}z_{ac})}{(N_{1} + N_{2})^{2}Z_{aa}Z_{df}} \right) \left(\frac{z_{bc} + z_{df}}{N_{1}} - \frac{z_{cb} + z_{fd}}{N_{2}} \right) \right] \quad (15)$$

$$\frac{E_{2}}{E_{s}} \approx \frac{N_{2}}{N_{1} + N_{2}} \left[1 + \frac{N_{1}z_{ab} - N_{2}z_{ac}}{(N_{1} + N_{2})Z_{aa}} + \left(\frac{N_{1}N_{2}(N_{1}z_{ab} + N_{2}z_{ac})}{(N_{1} + N_{2})^{2}Z_{aa}Z_{df}} \right) \right] \quad (16)$$

Equations (15) and (16) should be compared with equations (3) and (4). The winding-impedance error terms are multiplied by small factors, as one would expect. However, note the new error terms

$$[(z_{ac} - z_{ab})/Z_{aa} \text{ and } (N_1 z_{ab} - N_2 z_{ac})/(N_1 + N_2)Z_{aa}]$$

that result from unbalanced coupling to winding a. While these errors can be extremely small, they can, nonetheless, be just as important as the other errors, which can be even smaller. The better the symmetry of field and windings, the smaller this coupling error will be.

The Gibbings Transformer [11]

The circuits of Figs. 1b and 1c are similar, except that an extra winding is added in 1c to supply the drive. Similarly, adding such a winding to the circuit of Fig. 6 results in the Gibbings circuit, shown in Fig. 7. In the circuit of Fig. 1c, the open-circuit voltage ratio depends only upon a mutualinspedance

inductance ratio, and a two-stage circuit cannot improve on that. However, in bridge circuits it places winding impedances in series with the impedances being compared, so that it is unsuitable for low-impedance measurements.

In the bridge circuit of Fig. 1c, the approximate impedance ratio at null is '

$$\frac{Z_1}{Z_2} \approx \frac{N_1}{N_2} \left[1 + \frac{z_{32} - z_{31}}{Z_{33}} + \frac{z_{21}}{Z_2} - \frac{z_{12}}{Z_1} + \left(\frac{z_{31} - z_{32}}{Z_{33}} \right) \left(\frac{(N_1 + N_2)^2 Z_{33}}{N_3^2 (Z_1 + Z_2)} \right) \right]$$
(17)

Here we have three types of errors, the first of which is the open-circuit error due to unequal coupling.

$$\frac{Z_{31}}{Z_{32}} \approx \frac{N_1}{N_2} \left[1 + \frac{z_{32} - z_{31}}{Z_{33}} \right]$$
(18)









The next two terms take into account the impedance in series with Z_1 and Z_2 .

If

$$N_{1}/N_{2} = (Z_{1} + z_{12})/(Z_{2} + z_{21}), \text{ then}$$
$$\frac{Z_{1}}{Z_{2}} \approx \frac{N_{1}}{N_{2}} \left[1 + \frac{z_{21}}{Z_{2}} - \frac{z_{12}}{Z_{1}} \right]$$
(19)

The last term is the open-circuit error multiplied by a loading factor. It is caused by the increased effect of the primary-winding impedance as the circuit is loaded and the input current increases.



The Gibbings circuit, Fig. 7, produces many error terms, of which only the principal ones are shown here:

$$\begin{aligned} \frac{Z_1}{Z_2} &\approx \frac{N_1}{N_2} \Biggl[1 + \frac{z_{sc} - z_{sb}}{Z_{ss}} \\ &+ \Biggl(\frac{N_1 z_{sb} + N_2 z_{sc} - (N_1 + N_2) z_{sa}}{(N_1 + N_2) Z_{ss}} \Biggr) \\ & \Biggl(\frac{N_2 (z_{bc} + z_{df}) - N_1 (z_{cb} + z_{fd})}{(N_1 + N_2) Z_{df}} \Biggr) \\ &+ \Biggl(\frac{N_1 N_2 (N_1 z_{ab} + N_2 z_{ac})}{(N_1 + N_2)^3 Z_{df}} \Biggr) \Biggl(\frac{z_{cb} + z_{fd}}{Z_2} - \frac{z_{bc} + z_{df}}{Z_1} \Biggr) \Biggr]$$
(20)

The open-circuit error is not improved, and includes an additional term that is a function of the added transformer's balance. The series-impedance error, however, is greatly reduced, making this circuit much more suitable for low-impedance comparisons. Although when two leads are used to connect Z_1 to windings *a* and *b* separately, their impedances add to z_{ab} , z_{ue} , and z_{br} , nonetheless they introduce only a very small error. Thus, with the addition of a "yoke" transformer (as shown in Fig. 7) to reduce the error contributed by other leads connecting Z_1 , this circuit functions as a good four-terminal bridge [11].

It has been shown that the addition of a second transformer, or a second core and additional windings, can improve vastly the characteristics of three basic transformer connections. It can:

• reduce the effective impedance of one winding of the isolating transformer shown in Fig. 1a;

 reduce the winding-impedance error in the divider shown in Fig. 1b; and

• reduce the series-impedance error of the bridge shown in Fig. 1c.

However, the addition of a second transformer can never improve a ratio accuracy beyond the ability of two windings to be linked by the same flux. The open-circuit ratio of the simple circuit of Fig. 1c is just as good as the ratio of any two-stage device. This ratio is determined only by core permeability, and by core and winding symmetry.

It should also be noted that two-stage devices cannot increase power efficiency by reducing winding resistance or core loss. Thus, power engineers are interested in them only as measurement devices.

REFERENCES:

- Sze, W. C., "An Injection Method for Self-Calibration of Inductive Voltage Dividers," NBS Journal of Research, January-March 1968, (Vol. 72C, No. 1).
- Cutkosky, R. D., "Active and Passive Direct-Reading Ratio Sets for the Comparison of Audio-Frequency Admittances," IEEE Transactions on Instrumentation and Measurement, December 1964, (Vol. IM-13, No. 4); pg 243.
- Foord, T. R., Langlands, R. C., and Binnie, A. J., "Transformer-Ratio Bridge Network with Precise Lead Compensation," Proc. IEE (Eng), September 1963, (Vol. 110, No. 9).
- Hall, H. P., "The Measurement of Electrolytic Capacitors," General Radio Experimenter, June 1966, (Vol. 40, No. 6).
- Hill, J. J. and Deacon, T. A., "Theory, Design and Measurement of Inductive Voltage Dividers," Proc. IEE (Eng), May 1968, (Vol. 115, No. 5).
- Oatley, C. W. and Yates, J. G., "Bridges with Coupled Inductive Ratio Arms as Precision Instruments for the Comparison of Laboratory Standards of Resistance or Capacitance," Proc. IEE (Eng), March 1954, (Vol. 101); pg 91.
- Hill, J. J., and Miller, A. P., "An AC Double Bridge with Inductively Coupled Ratio Arms for Precision Platinum-Resistance Thermometry," Proc. IEE (Eng), Feb., 1963, (Vol. 110, No. 2); pg 453.
- McGregor, M. C., et al., "New Apparatus at NBS for Absolute Capacitance Measurement," IRE (IEEE) Transactions on Instrumentation, December 1968, (Vol. 1-7).
- Brooks, H. B., and Haltz, F. C., "The Two-Stage Current Transformer," AIEE Transactions, June 1922, (Vol. 41); pg 382.
- Deacon, T. A., and Hill, J. J., "Two-Stage Inductive Voltage Dividers," Proc. IEE (Eng), June 1968, (Vol. 115); pg 888.
- Gibbings, D. L. H., "An Alternating-current Analogue of the Kelvin Double Bridge," Proc. IEE (Eng), 1962, (Vol. 109C); pg 307.