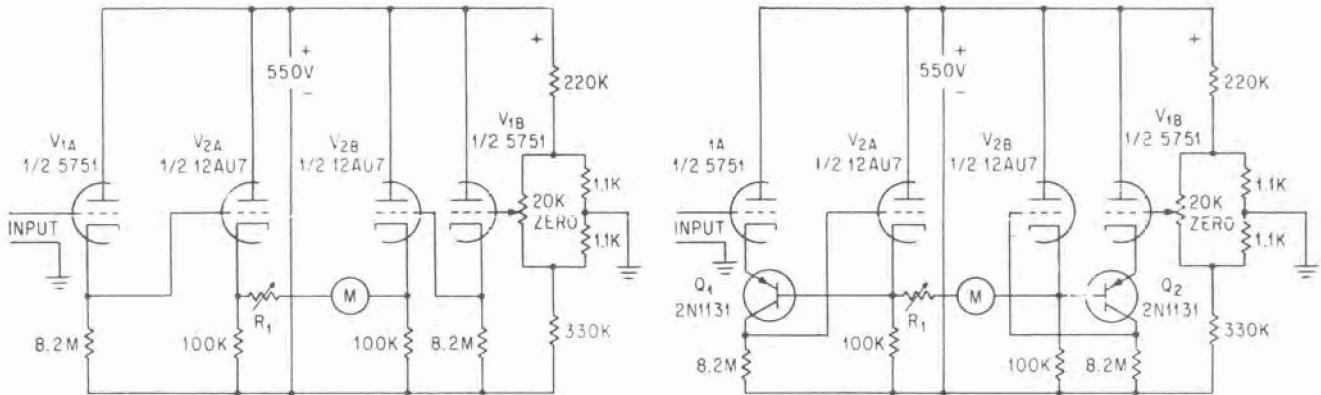




DHC



IMPEDANCE of meter drive circuit (left) depends on tube  $g_m$  and is subject to aging; hybrid circuit (right) uses transistors for below-1-ohm drive impedance, achieving independence from  $g_m$  variation

# HYBRID VOLTMETER Avoids Aging Errors

By JAMES J. FARAN Jr., General Radio Corp., West Concord, Mass.

Technique stabilizes drive circuits against changes in tube transconductance

**ONE REASON** why most vacuum-tube voltmeters require calibration at regular intervals is the aging, or change in transconductance, of the vacuum tubes. In this, a balanced vacuum-tube voltmeter uses transistors to bring vacuum-tube output impedances down to a small fraction of an ohm. The resulting performance is virtually independent of changes in tube  $g_m$ , and consequently the vtm rarely if ever requires recalibration.

The balanced vtm circuit, before modification, is shown in the left-hand illustration. Tube  $V_1$  operates at low plate current to

keep grid current small;  $V_2$  is operated at normal conditions to drive the meter circuit. Resistor  $R_1$  is switched to different values for various voltage ranges. The long-term stability of this circuit depends on constancy of voltage gain and on the output impedance of each side of the circuit. Voltage gain of  $V_1$  is highly stabilized at  $\mu/(\mu + 1)$  because of the large load resistance (8.2 megohms). The open-circuit voltage gain of  $V_2$  is also stabilized for the same reason, but its output resistance (approximately  $1/g_m$ ) increases steadily with life as  $g_m$  decreases.

**Example**—For a 1.5-volt range and with a 1-ma meter, the total multiplier resistance is a little smaller than 1,500 ohms. This is composed of the output resistance of each half of  $V_2$  (about 360

ohms each), the meter internal resistance, and  $R_1$ . Aging of the tubes to half their original  $g_m$  would double their output resistances and cause the meter to read 30 percent low on that range.

The addition of a transistor in each side of the circuit (right) reduces output impedance to a small fraction of an ohm. A decrease in the  $g_m$  of  $V_2$  to half its original value is now no longer important since the output impedance of each side of the circuit is still less than an ohm. The voltage gain of  $V_1$  is unaffected by the addition of the transistor because the input impedance at the emitter remains substantially unchanged. Voltage gain of the  $Q_1 - V_2$  combination is close to unity, and is highly stable.

Transistor requirements are modest. Base-to-collector voltage is simply the cathode-to-grid bias of  $V_2$ , a maximum of 6 volts. Collector current of  $Q_1$  and plate current of  $V_1$  are equal and quite low. There is no stiff requirement for current gain, so the transistor is used in what is effectively a grounded-base connection.

This hybrid circuit converts a normal good-quality voltmeter into a highly stable instrument, which should not require recalibration even at the normal end of life (half  $g_m$ ) of the vacuum tubes.

A 112 HYBRID VM.